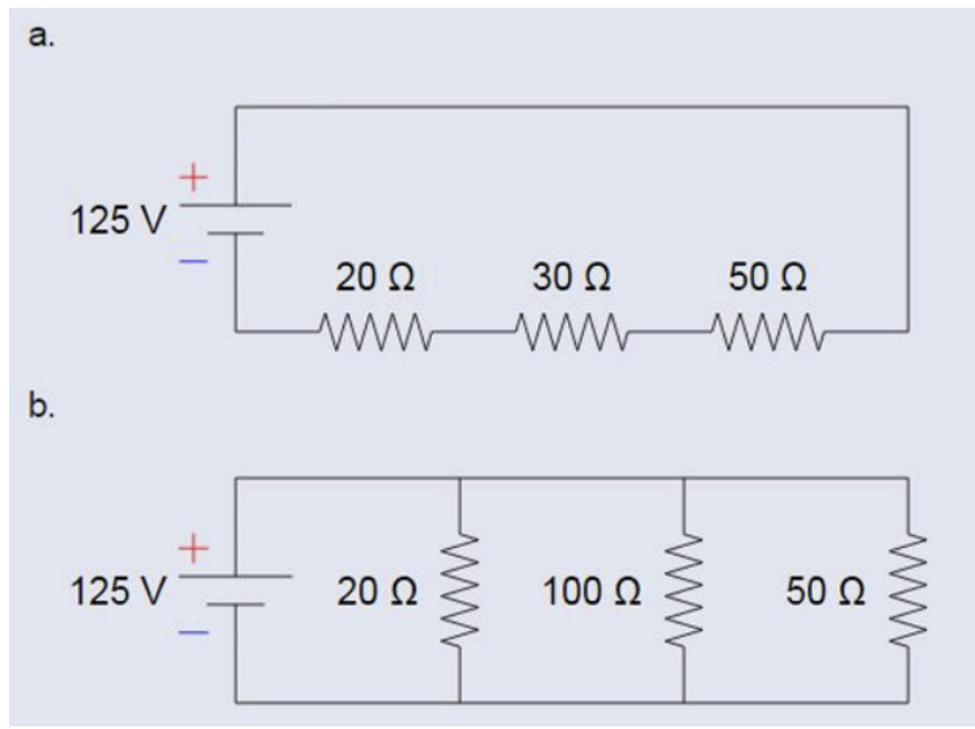


## Eric Macharia Muthii(166390) - Circuit Calculations



### 1. Calculate the total resistance in ohms.

Circuit A:

$$R_{\text{total}} = 20 + 30 + 50 = 100 \text{ ohms}$$

Circuit B;

$$1/R_{\text{total}} = 1/20 + 1/100 + 1/50 = 0.08$$

$$1/R_{\text{total}} = 1/0.08$$

$$R_{\text{total}} = 12.5 \text{ ohms}$$

### 2. Calculate the total current from the power supply

Circuit A;

$$I = V/R = 125/100 = 1.25 \text{ Amps}$$

Circuit B;

$$I = V/R = 125/12.5 = 10 \text{ Amps}$$

### 3. Calculate the current through each resistor

Circuit A;

Since the resistors are connected in series the current remains the same between all resistors which is **1.25 Amps**

Circuit B;

$$I_{20\Omega} = V/R = 125/20 = 6.25 \text{ Amps}$$

$$I_{100\Omega} = V/R = 125/100 = 1.25 \text{ Amps}$$

$$I_{50\Omega} = V/R = 125/50 = 2.5 \text{ Amps}$$

#### **4. Calculate the Voltage drop through each resistor**

Circuit A;

$$V_{20\Omega} = IR = 1.25 \times 20 = 25 \text{ V}$$

$$V_{30\Omega} = IR = 1.25 \times 30 = 37.5 \text{ V}$$

$$V_{50\Omega} = IR = 1.25 \times 50 = 62.5 \text{ V}$$

Circuit B;

Since the resistors are in parallel the voltage drop will be equal to the source voltage which is 125 volts

#### **5. Calculate the Power dissipated through each resistor (use Watt's Law: Power = Voltage \* Current)**

Circuit A;

$$P_{20\Omega} = VI = 25 \times 1.25 = 31.25 \text{ W}$$

$$P_{30\Omega} = VI = 37.5 \times 1.25 = 46.875 \text{ W}$$

$$P_{50\Omega} = VI = 62.5 \times 1.25 = 78.125 \text{ W}$$

Circuit B;

$$P_{20\Omega} = VI = 125 \times 6.25 = 781.25 \text{ W}$$

$$P_{100\Omega} = VI = 125 \times 1.25 = 156.25 \text{ W}$$

$$P_{50\Omega} = VI = 125 \times 2.5 = 312.5 \text{ W}$$